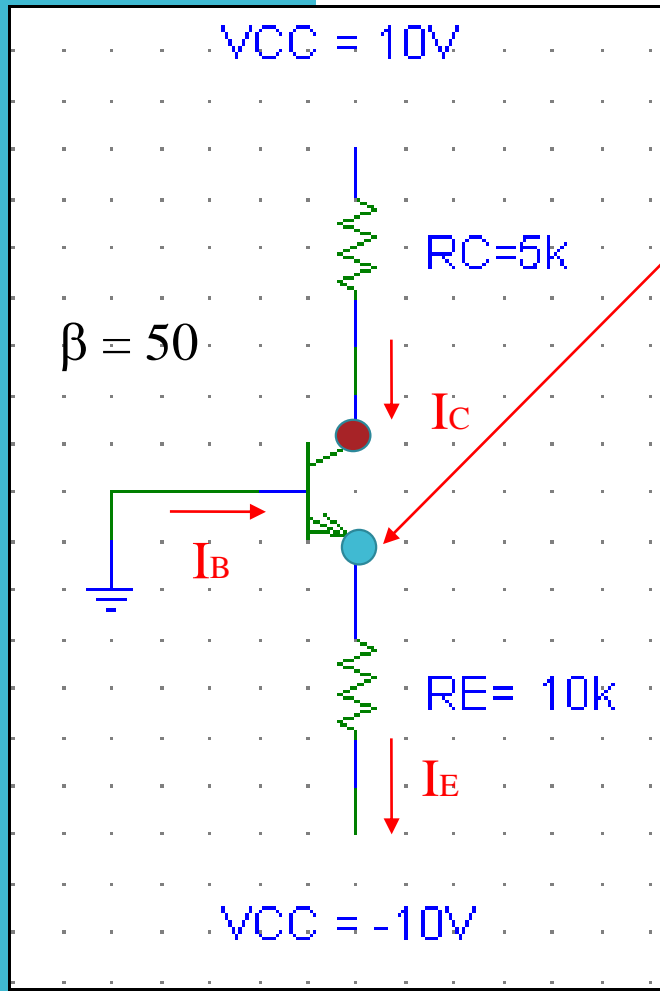


Διπολικά Transistor

18/1/2021

Άσκηση 1



$$V_E = 0 - 0.7 = -0.7V$$

$$I_E = (V_E - (-10))/R_E = (-0.7 + 10)/10K = 0.93mA$$

$$I_C \approx I_E = 0.93mA$$


$$I_C = \beta I_B + (\beta + 1) I_{CBO} \text{ και συνεπώς (o = open)}$$

$$I_B = I_C/\beta = (0.93/50) mA = 18.6\mu A$$

$$V_C = 10 - I_C R_C = 10 - 0.93(5) = 5.35V \text{ (κόκκινο σημείο)}$$

$$V_{CE} = 5.35 - -0.7 = 6.05V$$

Άσκηση 2

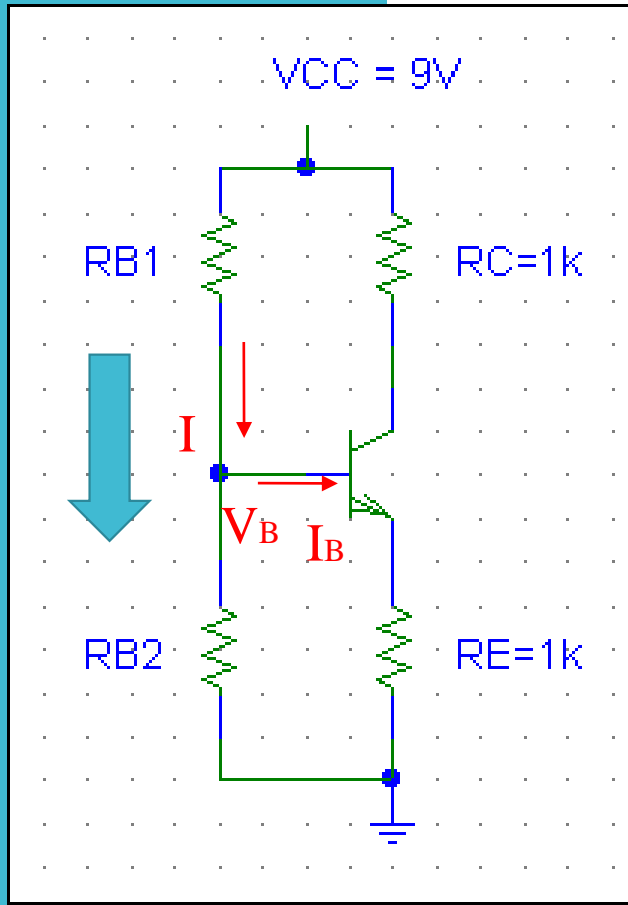

• Έστω $V_B = 3V$ και $I = 0.2mA$. Να υπολογίσετε τις αντιστάσεις του διαιρέτη τάσης

(a) R_{B1} και R_{B2} αποτελούν διαιρέτη ρεύματος

Υποθέτουμε ότι $I \gg I_B$ $I = V_{CC}/(R_{B1} + R_{B2})$

$$0.2(mA) = 9 / (R_{B1} + R_{B2})$$


και

$$V_B = V_{CC} [R_{B2}/(R_{B1} + R_{B2})]$$

$3 = 9 [R_{B2}/(R_{B1} + R_{B2})]$, Λύνοντας ως προς R_{B1} και R_{B2} .

$$R_{B1} = 30K\Omega, \text{ και } R_{B2} = 15K\Omega.$$

Άσκηση 3

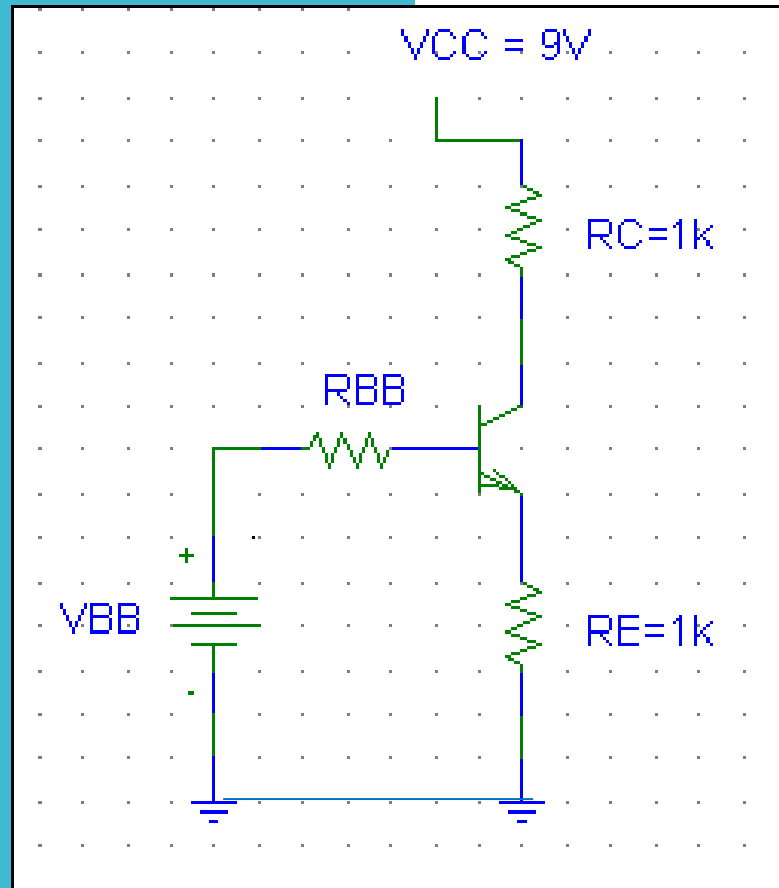

Σημείο λειτουργίας του BJT


- Χρησιμοποιώ το Thevenin

- Makes the circuit simpler

- $V_{BB} = V_B = 3V$

- $R_{BB} = R_{B1} || R_{B2} = 30K\Omega || 15K\Omega = .10K\Omega$

Λύση με βρόχους

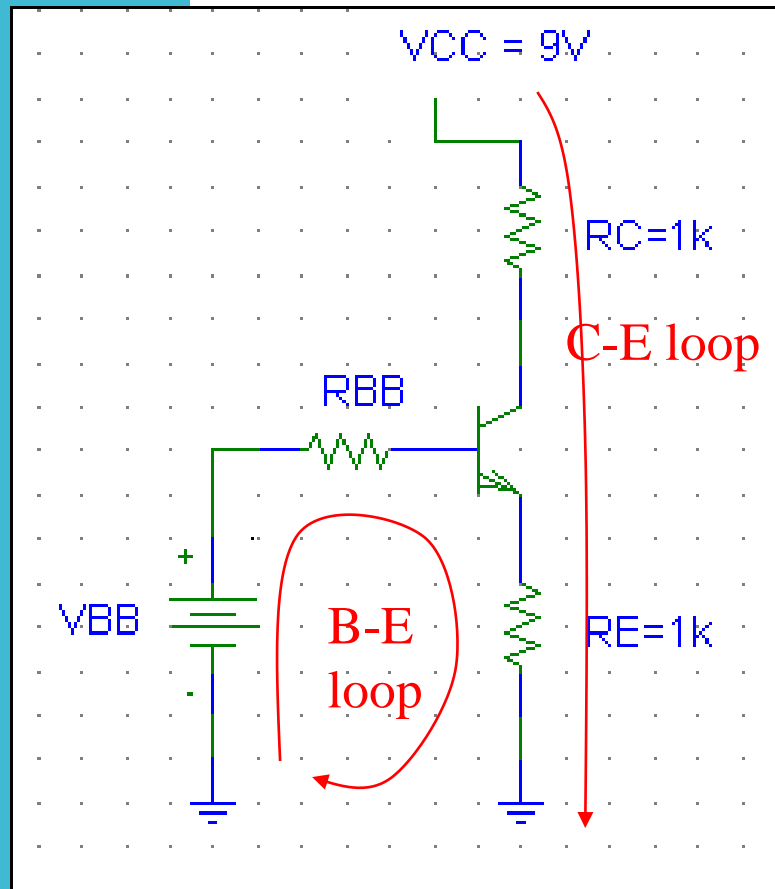

B-E βρόχος


$$V_{BB} = I_B R_{BB} + V_{BE} + I_E R_E$$

C-E βρόχος

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

Λύνουμε ως προς I_C , V_{CE} , και I_B .

Παράδειγμα

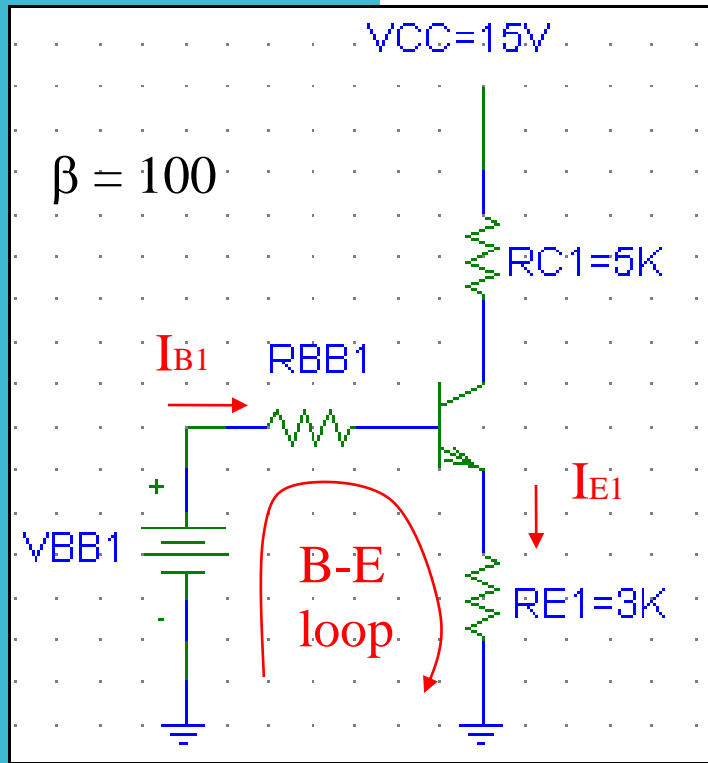

- $R_{BB1} = R_{B1} || R_{B2} = 50 || 100 = 33K$

- $V_{BB1} = V_{CC} [R_{B2} / (R_{B1} + R_{B2})]$

$$V_{BB1} = 15 [50K / 150K] = 5V$$

Βήμα 1

- B-E βρόχος

$$V_{BB1} = I_{B1} R_{BB1} + V_{BE} + I_{E1} R_{E1}$$


Εάν έστω $I_{B1} \approx I_{E1} / \beta$

$$5 = I_{E1} 33K / 100 + 0.7 + I_{E1} 3K$$


και συνεπώς: $I_{E1} = 1.3mA$

Αν θέλω μπορώ να βρω και το I_{B1}

Κύκλωμα
διπλών BJT
(NPN και PNP)

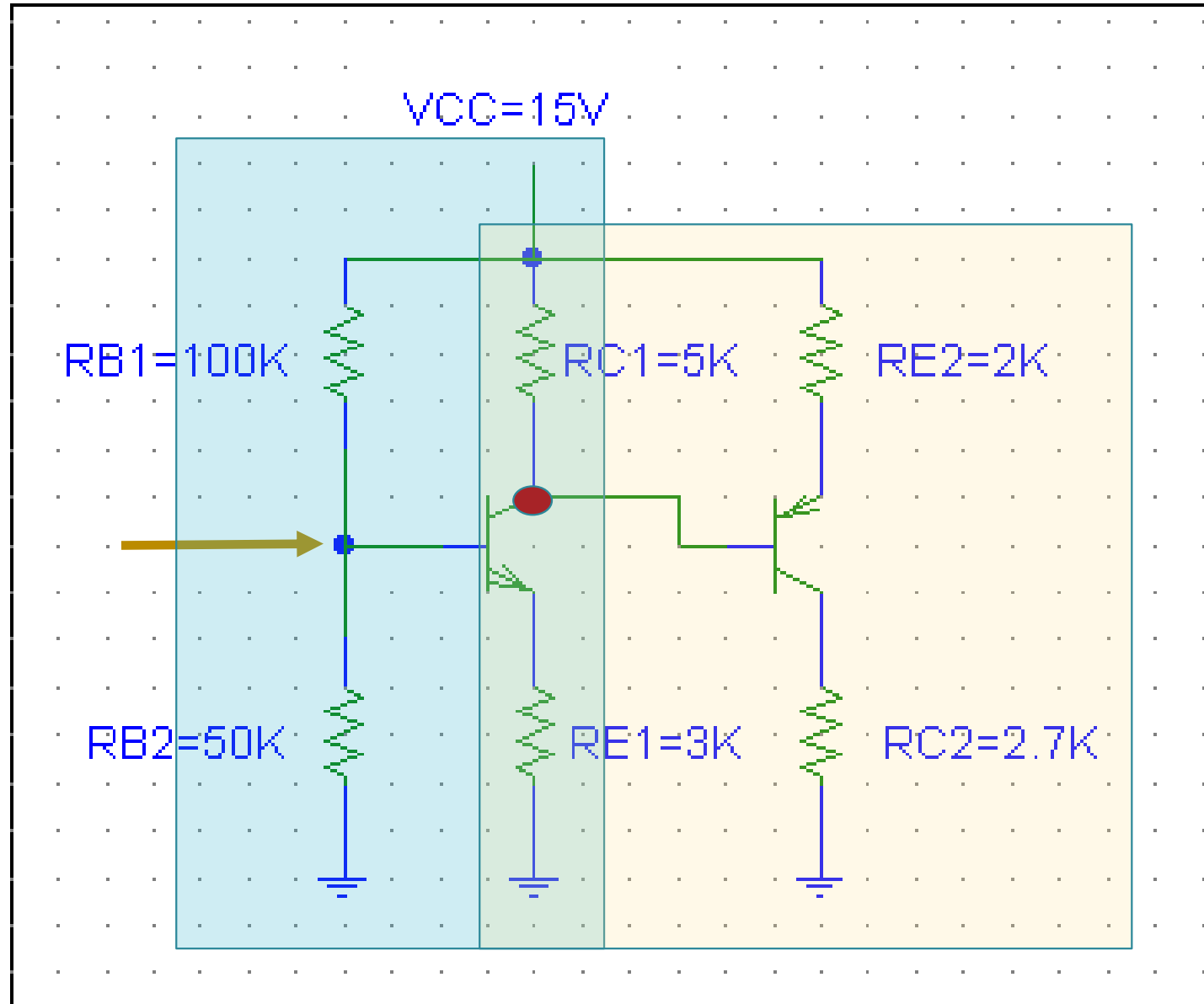

Παράδειγμα

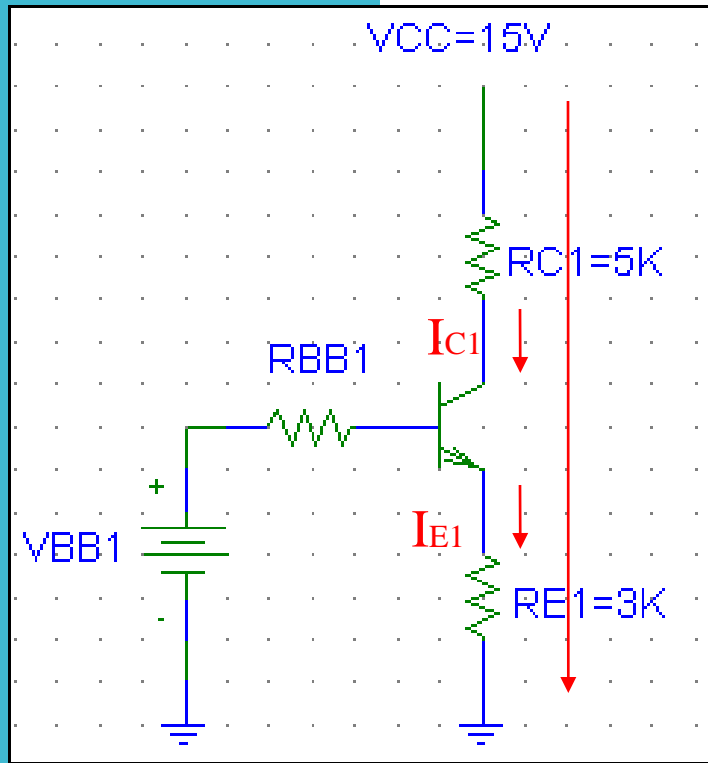

C-E βρόχος


$$V_{CC} = I_{C1} R_{C1} + V_{CE1} + I_{E1} R_{E1}$$

$$15 = 1.3(5) + V_{CE1} + 1.3(3)$$


$$V_{CE1} = 4.87V$$

Το αρχικό κύκλωμα της σελ.7

Παράδειγμα

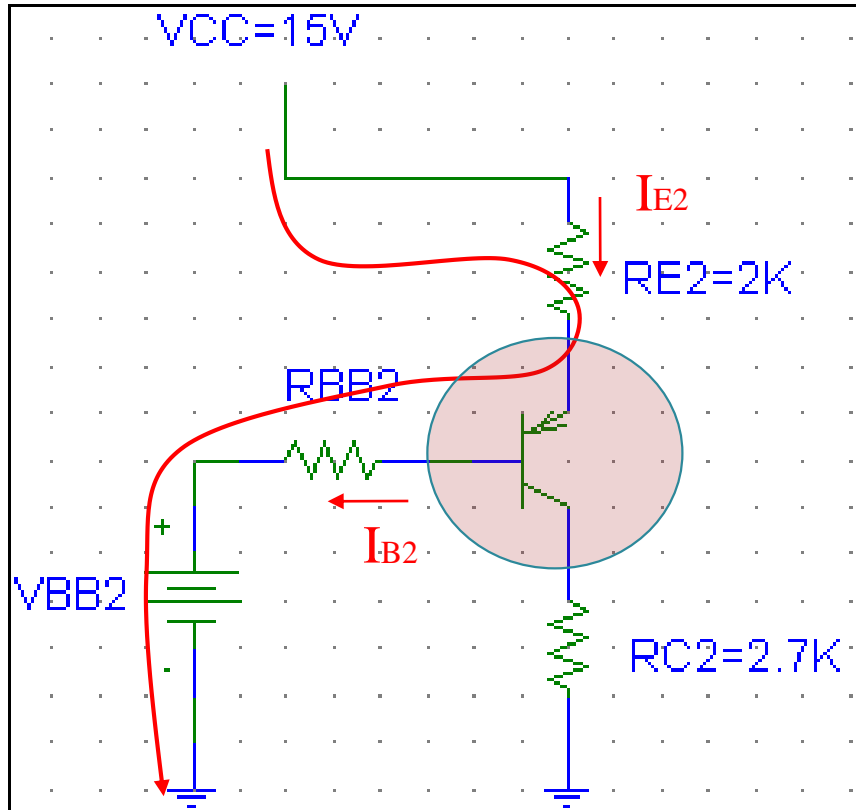

• B-E βρόχος

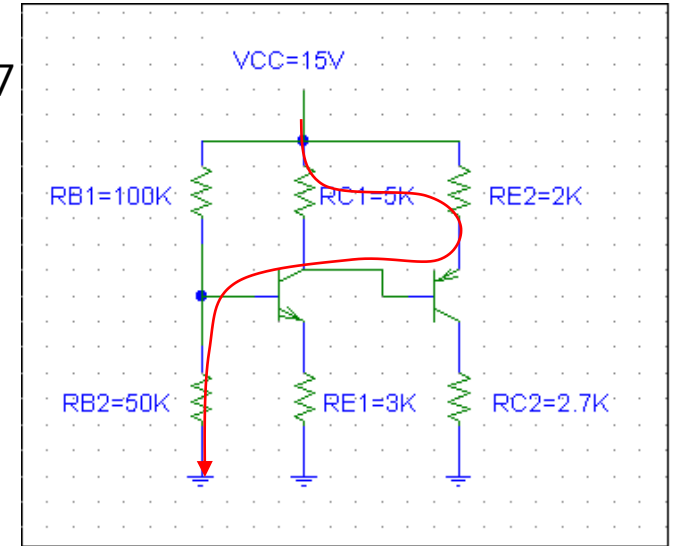

$$V_{CC} = I_{E2}R_{E2} + V_{EB} + I_{B2}R_{BB2} + V_{BB2}$$


$$15 = I_{E2}(2K) + .7 + I_{B2}(5K) + 4.87^* + 1.3mA(3K)$$

$$I_{B2} \approx I_{E2} / \beta, \text{ και λύνω ως προς } I_{E2}$$

$$I_{E2} = 2.8mA$$

* Βλέπε σελ.8

Παράδειγμα

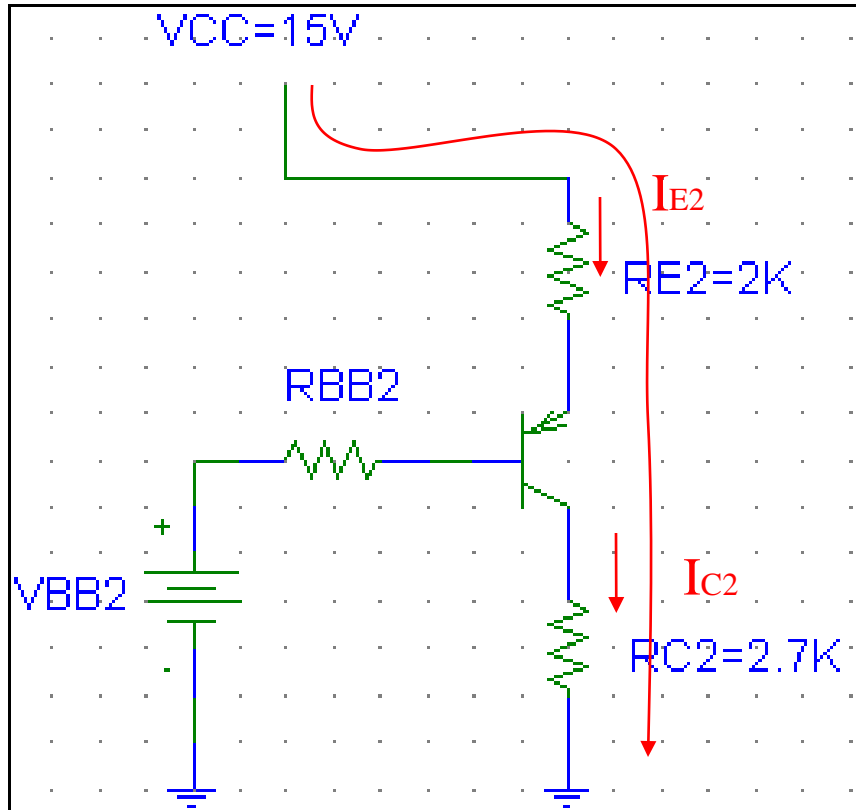

Βήμα 2

•C-E βρόχος



$$V_{CC} = I_{E2}R_{E2} + V_{EC2} + I_{C2}R_{C2}$$

$$15 = 2.8(2) + V_{EC2} + 2.8(2.7)$$


Λύνοντας ως προς V_{EC2}

$$V_{CE2} = 1.84V$$


(PNP)

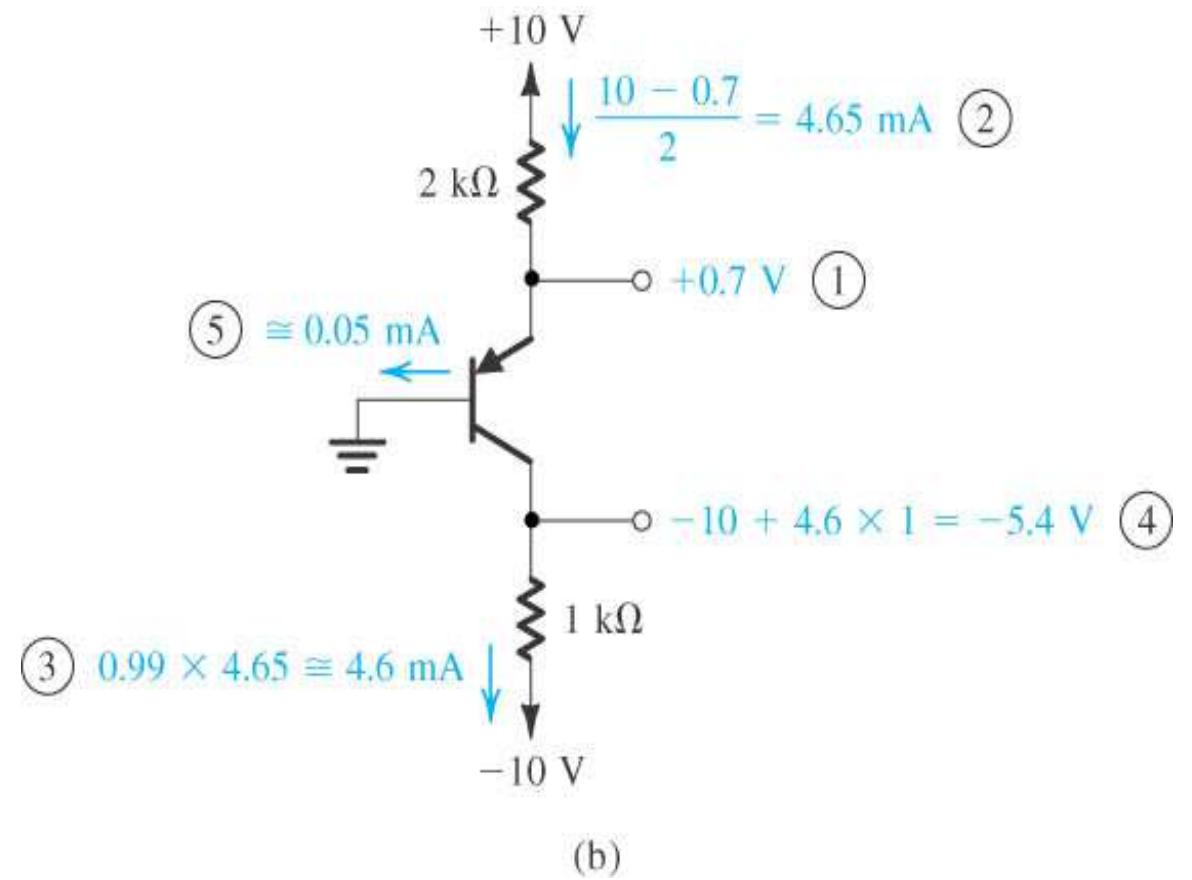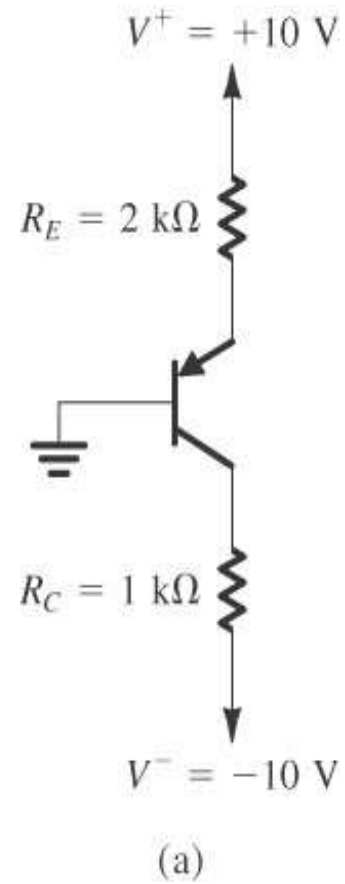

$\beta=100$

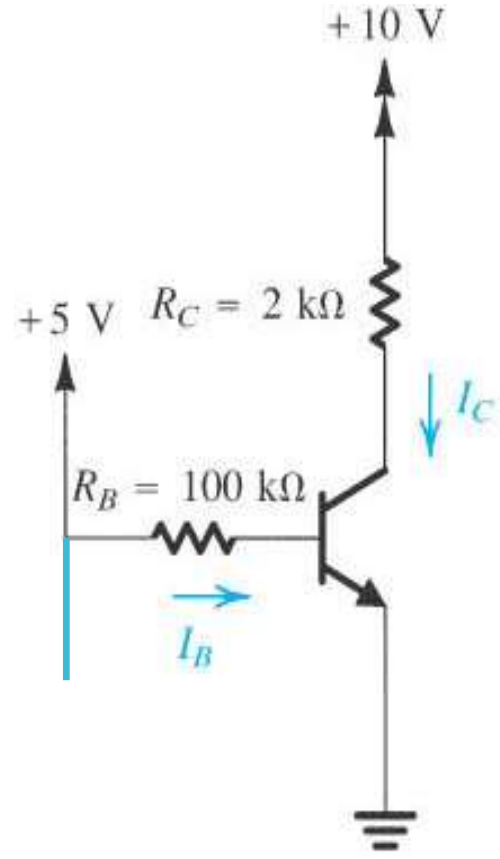


(a)

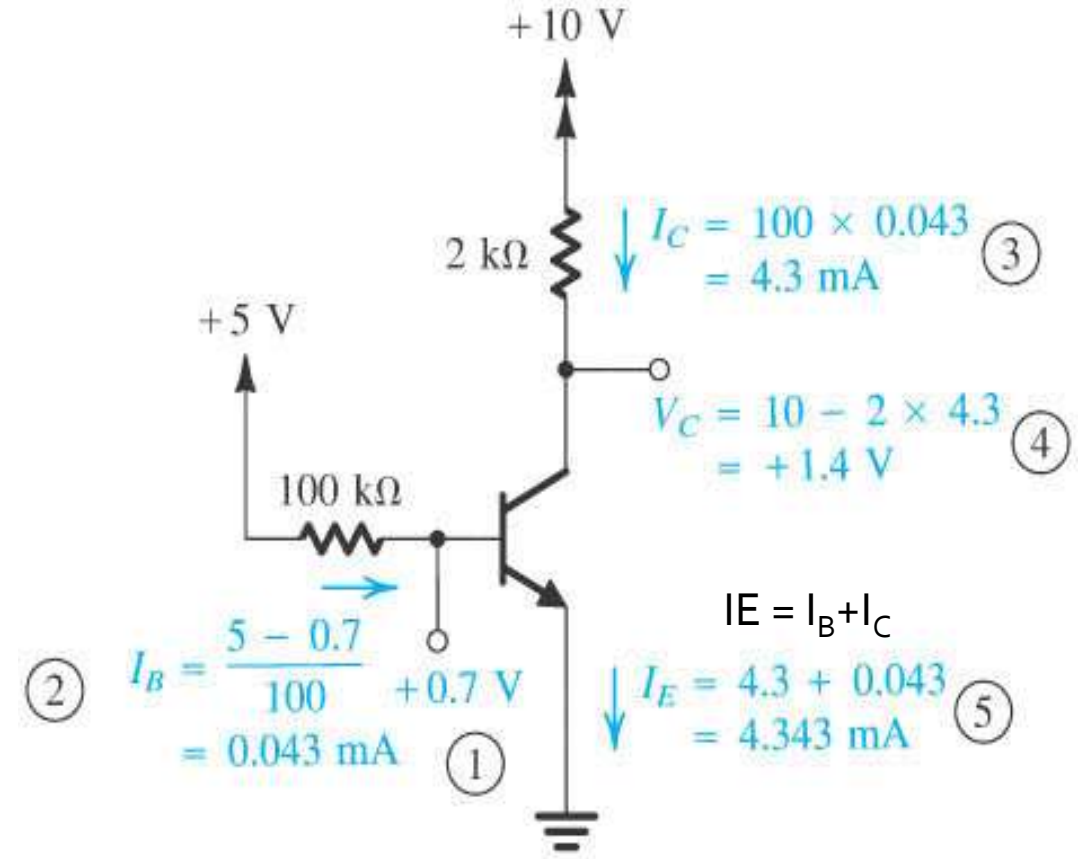


(b)

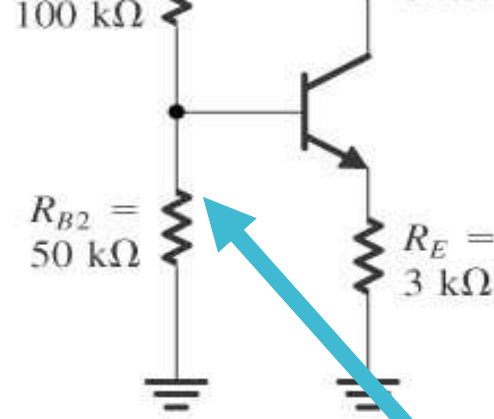
$$V_{BB} = \frac{R_{B2}}{R_{B1} + R_{B2}} * V_{CC} = \frac{50}{150} * 15 = 0.33 * 15 V = 5V$$




(a)

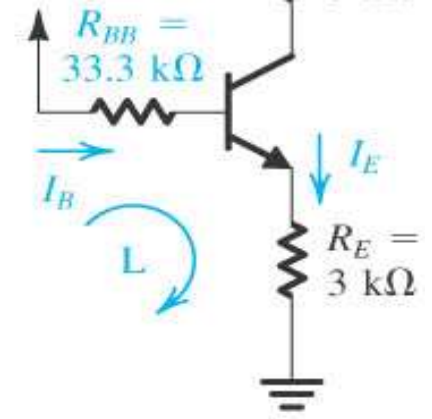


(b)

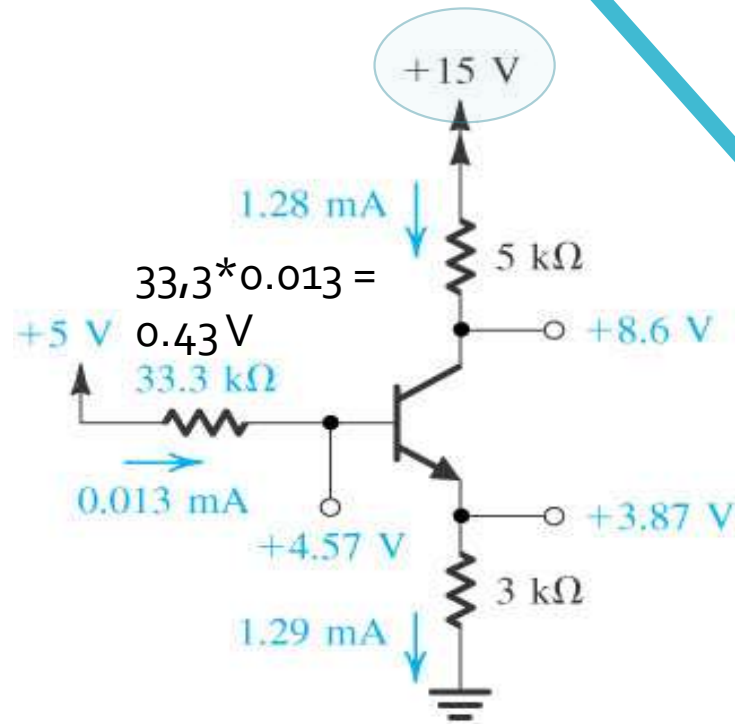


(c)


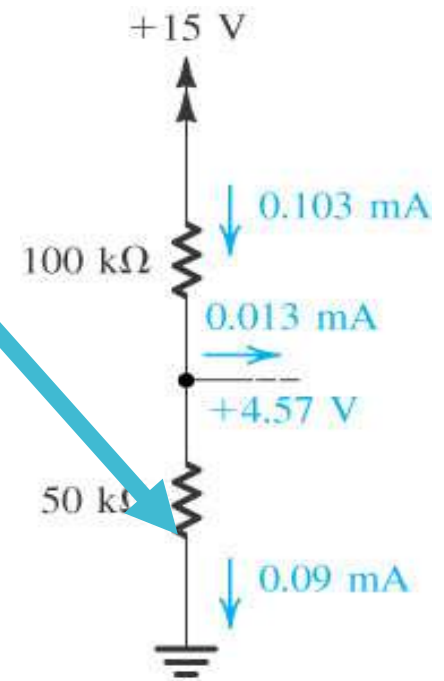


(d)

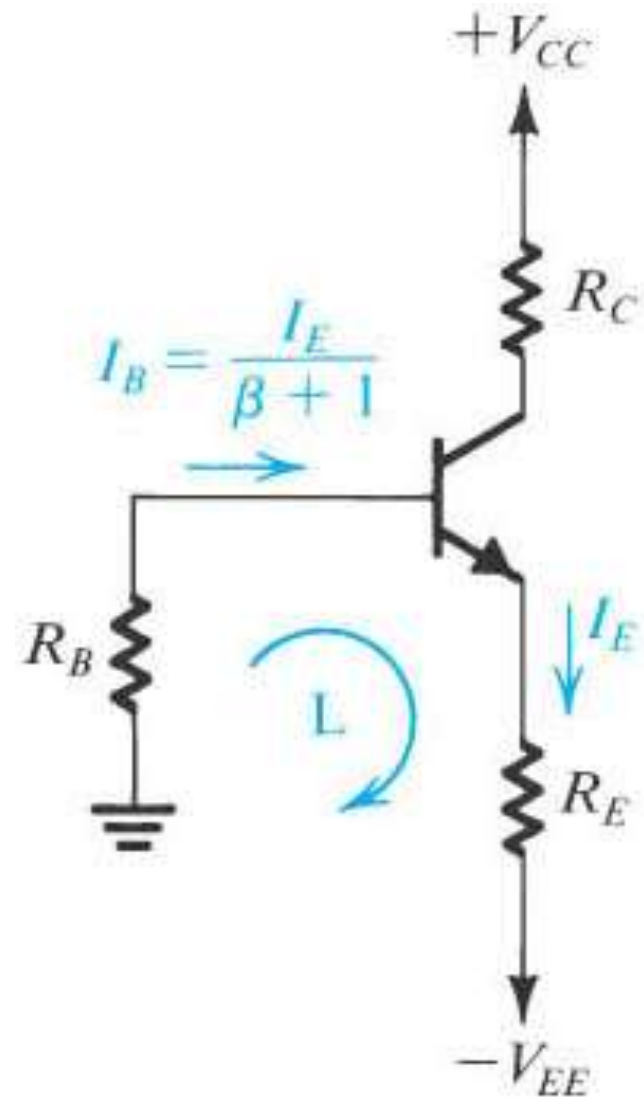


Ανάδραση

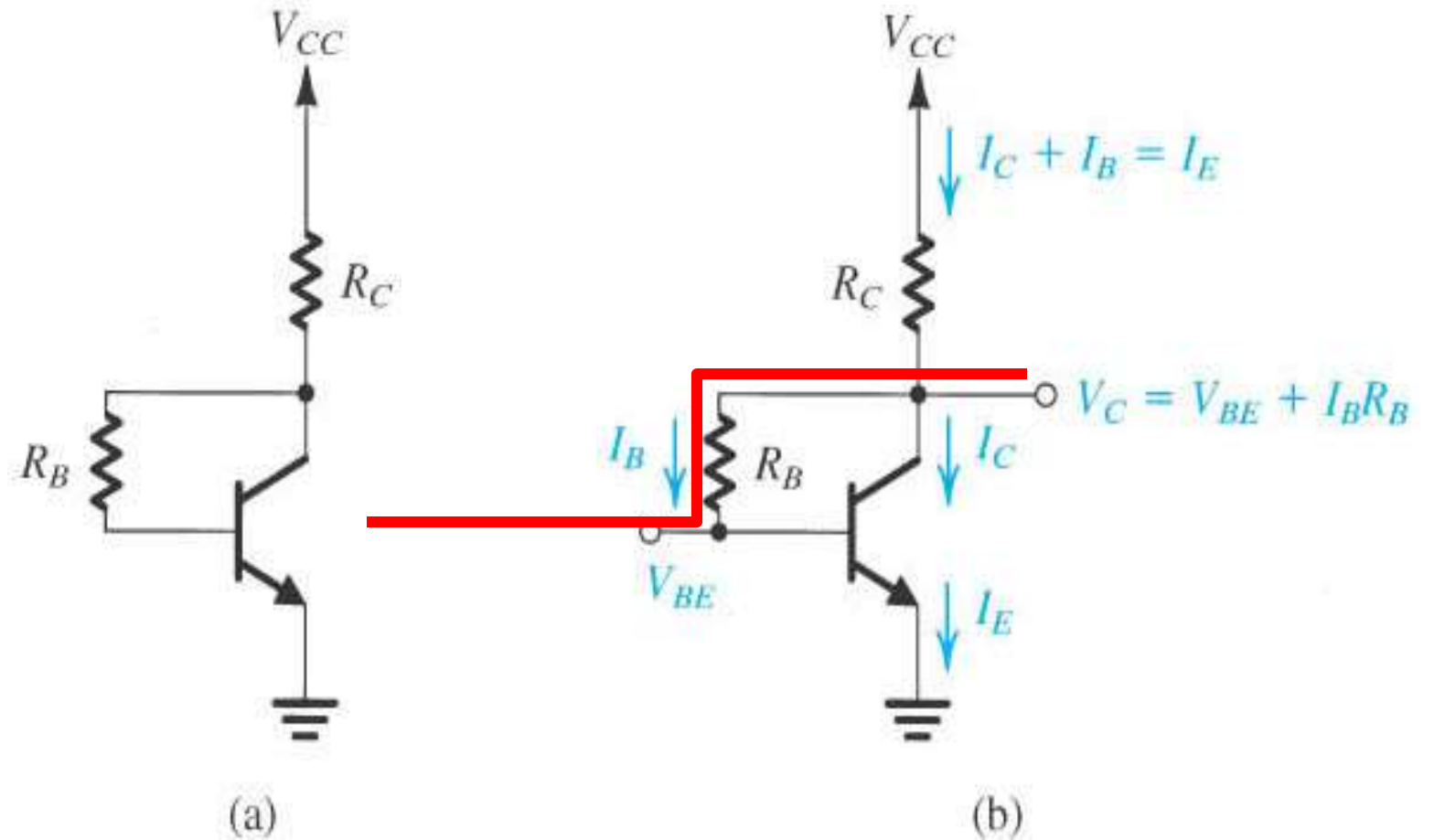

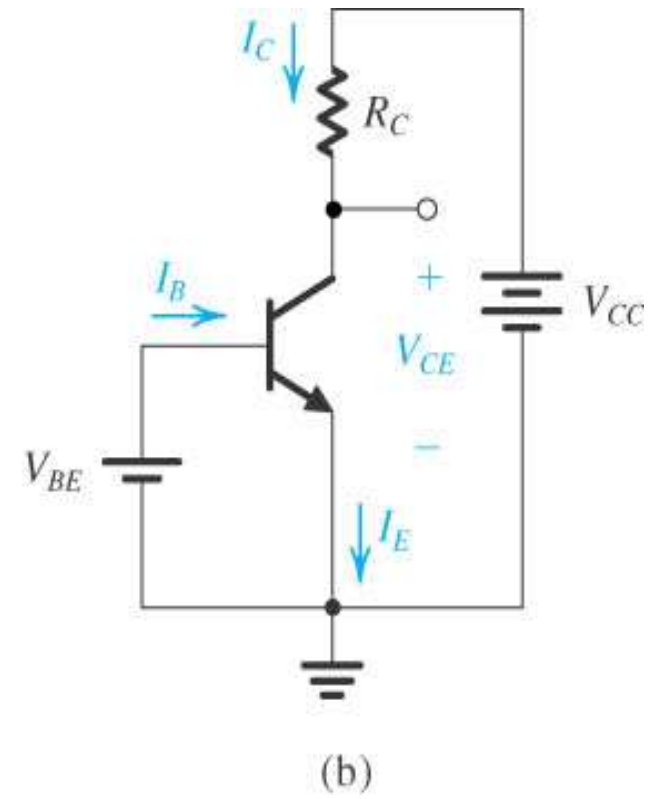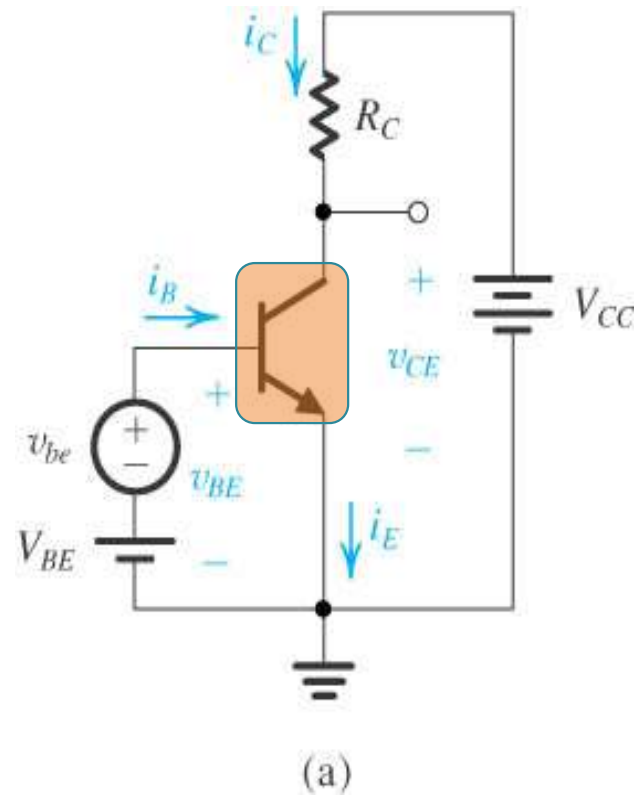

Παράδειγμα

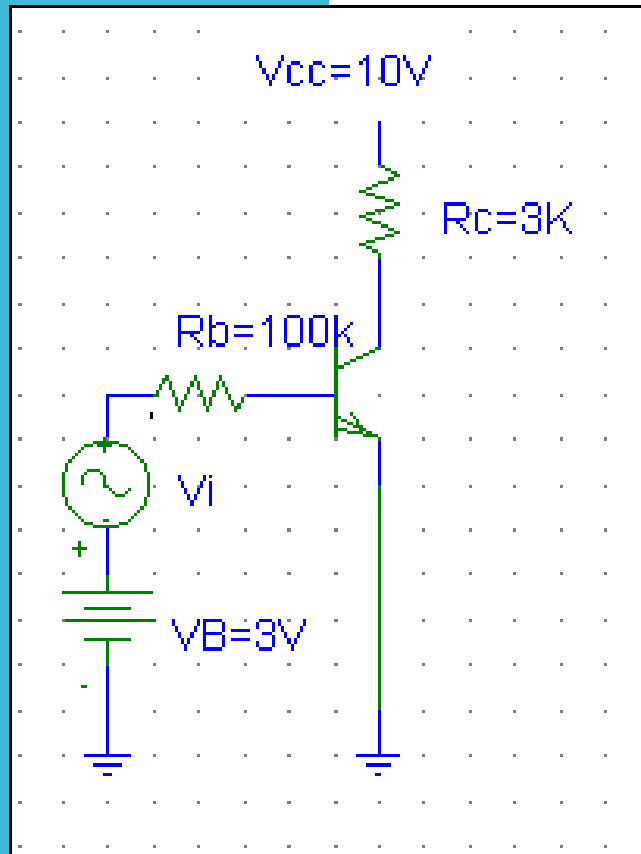Να υπολογίσετε το v_{out}/v_{in} , (Δίνεται $\beta = 100$)



DC problem

Να υπολογίσετε τα I_C και V_{CE}

B-E βρόχος

$$3 = I_B R_B + V_{BE}$$

$$I_B = (3 - 0.7) / R_B = 0.023 \text{ mA}$$

C-E βρόχος



$$V_{CE} = 10 - I_C R_C$$

$$V_{CE} = 10 - (2.3)(3)$$

$$V_{CE} = 3.1 \text{ V}$$

Q σημείο: $V_{CE} = 3.1 \text{ V}$,
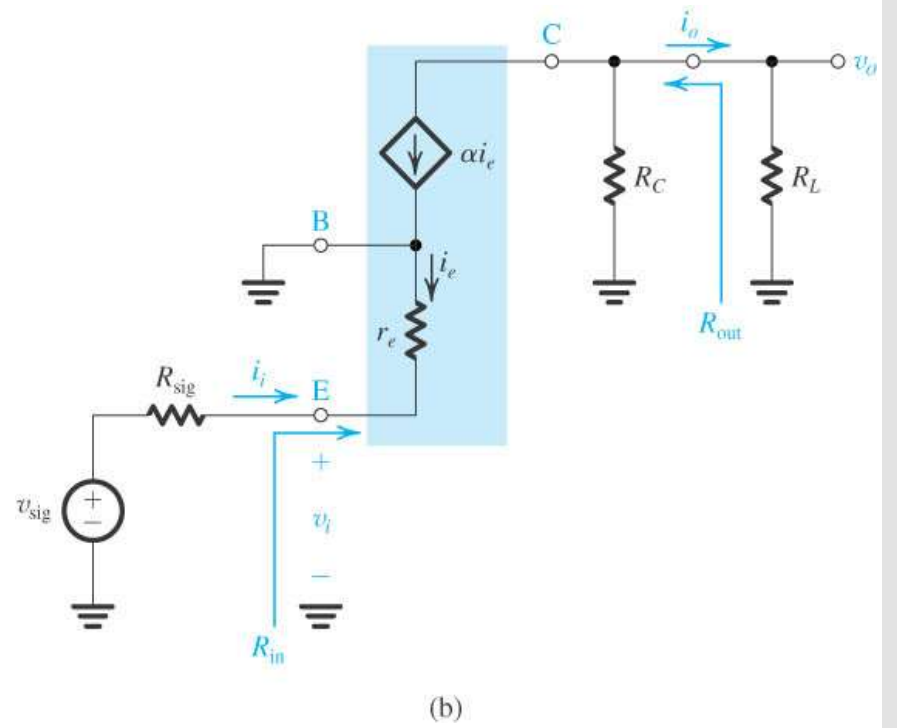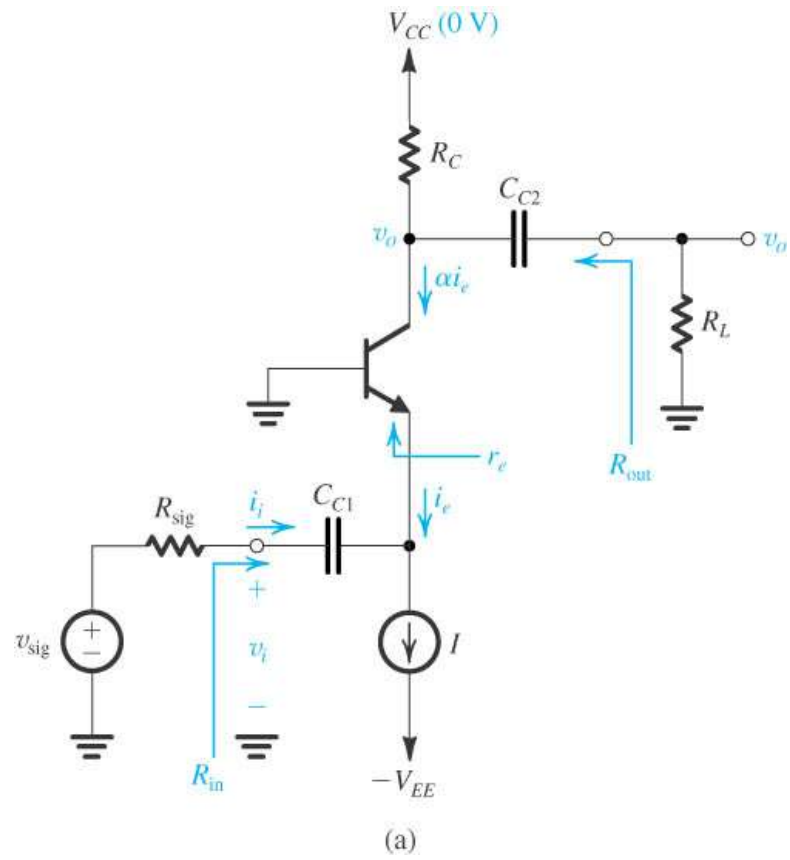
$$*I_C = 2.3 \text{ mA} = (100 * 0.023) (\beta * I_B)$$



Ανάλυση
μεγάλου
σήματος

