

Υπολογιστικά Συστήματα Υψηλής Αξιοπιστίας

Πανεπιστήμιο Δυτικής Αττικής

Ακαδημαϊκό έτος 2019-2020

Παρουσίαση 1^η:

**Εισαγωγή στον Έλεγχο Ολοκληρωμένων κυκλωμάτων
(Integrated circuit Testing)**

Σκοπός παρουσίασης


- Να παρουσιάσει θέματα που σχετίζονται με τον έλεγχο IC (IC testing) και τη σχετική τεχνολογία
- Έμφαση στα εξής:
 - Σημασία του ελέγχου στη διαδικασία σχεδιασμού και κατασκευής
 - Προκλήσεις στο test generation και το fault modeling

Περιεχόμενα

- Introduction
- Testing During VLSI Life Cycle
- Test Generation
- Fault Models
- Test Technology

Introduction

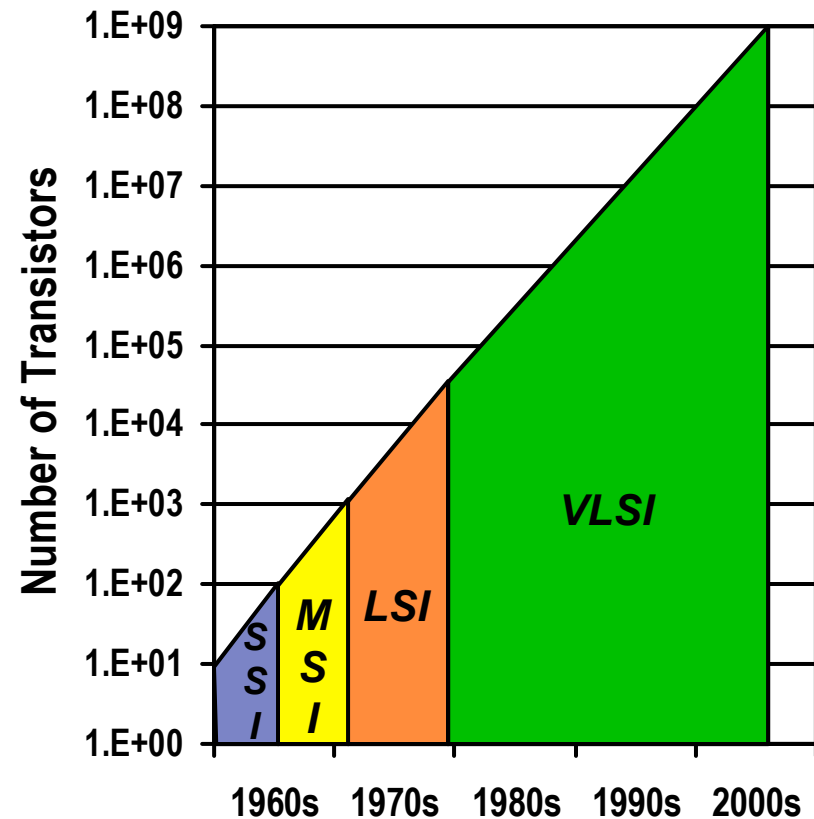- Integrated Circuits (ICs) have grown in size and complexity since the late 1950's
 - Small Scale Integration (SSI)
 - Medium Scale Integration (MSI)
 - Large Scale Integration (LSI)
 - Very Large Scale Integration (VLSI)
- *Moore's Law*: scale of ICs doubles every 18 months
 - Growing size and complexity pose new testing challenges



Σημασία του Ελέγχου (1)

- ❑ Decreasing feature size (dimensions)
 - from μm => nm for
 - transistors
 - interconnecting wires
- ❑ Operating frequencies have increased
 - from 100KHz => several GHz
- ❑ Decreasing feature size increases probability of defects during manufacturing process
 - A single faulty transistor or wire results in faulty IC
- ❑ Hence, testing required
 - to guarantee fault-free products


Σημασία του Ελέγχου (2)

- *Rule of Ten*: cost to detect faulty IC increases **by an order of magnitude** as we move from:
 - device → PCB → system → field operation
 - Testing performed at each of these levels
- Testing required during:
 - Manufacturing
 - to improve yield
 - Field operation to:
 - ensure fault-free system operation
 - initiate repairs when faults are detected

Ορισμός του Ελέγχου

□ Testing consists of

 - Applying Input test stimuli to Inputs of *circuit under test* (CUT), and
- Analyzing output responses
 - If correct (pass), CUT assumed to be fault-free
 - If incorrect (fail), CUT assumed to be faulty




Κύκλος ανάπτυξης IC

□ Design error

- Discovered during design verification
- Corrections made prior to fabrication


□ Manufacturing error (Defect)

 - a flaw or physical imperfection that can lead to a fault
- Discovered during Fabrication, Packaging, ...



Design Verification

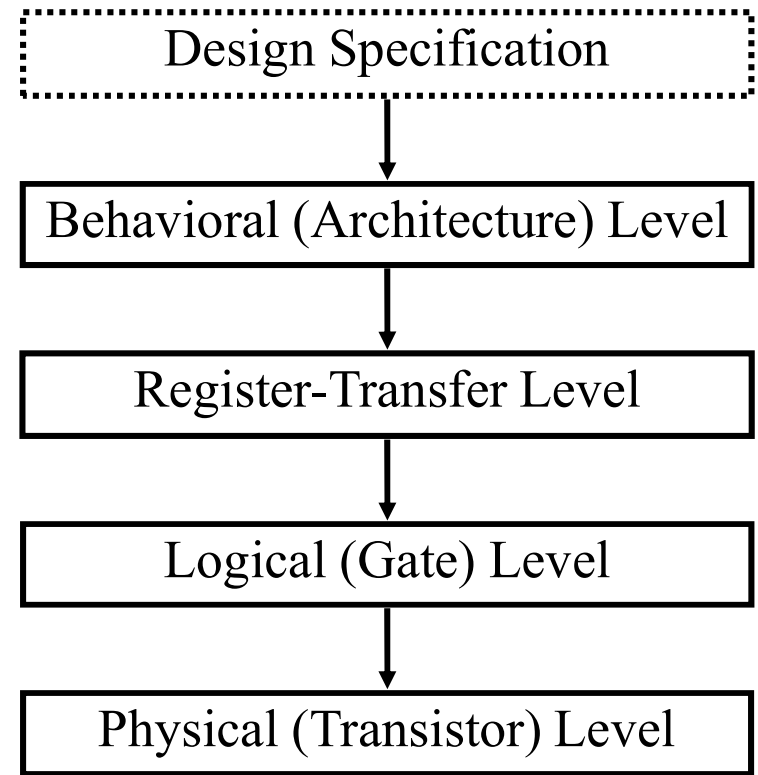- Different levels of abstraction
- RTL to physical level
 - CAD tools
- Simulation used at various level to test
 - For design errors
 - If the design meets system timing requirements after synthesis



Yield and Reject Rate

□ Faulty chips due to manufacturing defects ☹️

- the % of good chips:

□ Yield loss ☹️

$$yield = \frac{\text{number of acceptable parts}}{\text{total number of parts fabricated}}$$

□ 2 types of yield loss


- Catastrophic – due to random defects
- Parametric – due to process variations

□ Undesirable situations during testing

- Faulty chip appears to be good (passes test)
- Good chip appears to be faulty (fails test)
 - Due to overstress during test

PCBs & Electronic Systems

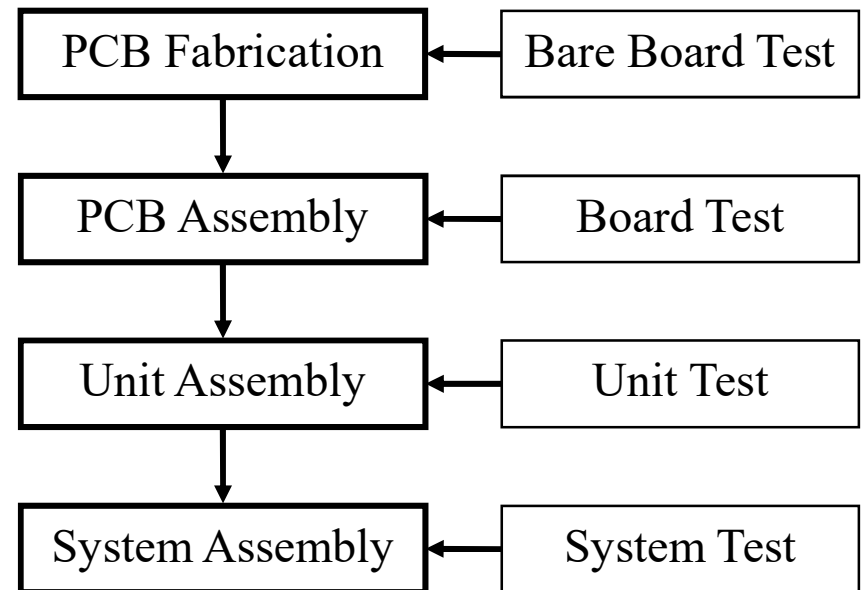- A system consists of PCBs that consist of ICs
- PCB fabrication similar to IC fabrication
 - Susceptible to defects
- Assembly steps also susceptible to defects
 - Testing performed at all stages of manufacturing
- Τι είναι πιο εύκολο;
 - Ο έλεγχος των PCBs?
 - Ο έλεγχος των ICs?



Είδη ελέγχου

□ Off-line testing

- while system (or portion of it) is taken out of service
- Performed periodically during low-demand periods
- Used for diagnosis (identification and location) of faulty replaceable components to improve repair time

□ On-line testing

- concurrent with system operation


Test Generation

- During testing, a sequence of test patterns, called *test vectors*, is applied to the CUT whose outputs are monitored and analyzed for the correct response
- *Fault coverage* is a quantitative measure of the quality of a set of test vectors
- Brute-force idea: Exhaustive testing – applying all possible test patterns to CUT
 - Is it practical?

Quiz (1)

Έστω το ακόλουθο κύκλωμα.


 
- Είναι συνδυαστικό ή ακολουθιακό;
- Πόσες εισόδους έχει;
- Πόσοι κύκλοι ρολογιού απαιτούνται για εξαντλητικό έλεγχο;



Quiz (2)

Έστω το κύκλωμα.

 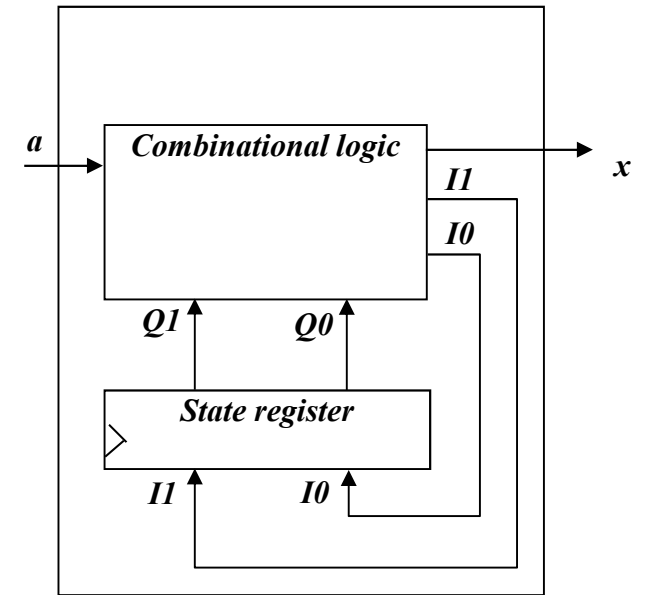- Είναι συνδυαστικό ή ακολουθιακό;
- Πόσες εισόδους έχει;
- Σχεδιάστε το διάγραμμα καταστάσεων του κυκλώματος
- Πόσοι κύκλοι ρολογιού απαιτούνται για εξαντλητικό έλεγχο;



Quiz (3)

1. Έστω ένα συνδυαστικό κύκλωμα που λειτουργεί στα 100KHz. Πόσος χρόνος απαιτείται για εξαντλητικό έλεγχο αν έχει:
 - 10 εισόδους
 - 20 εισόδους
 - 60 εισόδους
2. Έστω ένα ακολουθιακό κύκλωμα που λειτουργεί στα 100KHz. Πόσος χρόνος απαιτείται για τον εξαντλητικό έλεγχο αν έχει:
 - 10 εισόδους και status register με 10 flip flop
 - 20 εισόδους και status register με 40 flip flop

Test Generation (1)


- **Goal:** Εύρεση συνόλου από set of test vectors με μέγιστη κάλυψη ελαττωμάτων (fault coverage)
 - Τι είναι η «**Κάλυψη ελαττωμάτων**»;
- Για να προσομοιώσουμε τη συμπεριφορά των ελαττωμάτων απαιτείται μοντέλο ελαττωμάτων (fault model)
- Για να αποφασίσουμε για το fault coverage χρησιμοποιούμε προσομοίωση ελαττωμάτων (Fault simulation)

Test Generation (2)

- Ένα καλό fault model:
 - Είναι computationally efficient for simulation
 - Περιγράφει με ακρίβεια τη συμπεριφορά των defects
- Κανένα fault model δεν είναι καλό για όλα τα defects ☹


Fault Model

 - Μια υπόθεση για τα σφάλματα (faults) που μπορούν να συμβούν
- Παραδείγματα:
 - Ένα καλώδιο να είναι «κολλημένο» στο 0
 - Ένα καλώδιο να καθυστερήσει να πάει από το 0 στο 1



Fault Models

 
- Ένα fault model έχει συνήθως 2 είδη faults
 - Π.χ. καλώδιο κολλημένο στο 0 ή κολλημένο στο 1
- Ένα κύκλωμα έχει n fault sites
- Διακρίνουμε Single faults και Multiple Faults
- Single faults: θεωρούμε ότι το κύκλωμα έχει 1 fault
 - Το πλήθος των single faults: $2 \times n$



$2 \times 2 = 4$ λάθη
Ποια είναι αυτά;

Fault Models

 - Multiple fault model: το κύκλωμα μπορεί να έχει πολλαπλά faults (συμπεριλαμβάνονται τα single faults)
 - Number of multiple fault = $3^n - 1$
 - Κάθε «σημείο» μπορεί να έχει λάθος ή να είναι fault-free
 - The “-1” represents the fault-free circuit
 - Μη πρακτικό λόγω του πλήθους των faults
- Συνήθως, καλό single fault coverage δίνει καλό multiple fault coverage



$3^2 - 1 = 8$ λάθη, ποια είναι;

Equivalent Faults & fault collapsing

□ Equivalent faults


- Ένα ή περισσότερα single faults που έχουν ίδια συμπεριφορά για όλους τους συνδυασμούς εισόδων
- Μόνο ένα fault από το σύνολο των equivalent faults χρειάζεται να προσομοιωθεί

□ Fault collapsing

- Removing equivalent faults
 - Except for one to be simulated
- Μειώνει το πλήθος των faults και άρα
 - το χρόνο για fault simulation
 - το χρόνο για test pattern generation

Stuck-at Faults

 - Any line can be
 - Stuck-at-0 (SA0)
 - Stuck-at-1 (SA1)
- Πώς επηρεάζει ένα fault π.χ.
 - a-SA0?
 - a-SA1?
- Πώς φτιάχνω το διπλανό πίνακα;




Truth table for fault-free behavior

$x_1x_2x_3$	000	001	010	011	100	101	110	111
y	0	1	0	0	0	1	1	1
a SA0	0	1	0	0	0	1	0	0
a SA1	0	1	1	1	0	1	1	1

Stuck-at Faults

Ερωτήματα:

 1. Πώς μπορώ να ανακαλύψω το a-SA0?
2. Πώς μπορώ να ανακαλύψω το a-SA1?



Truth table for fault-free behavior


$x_1x_2x_3$	000	001	010	011	100	101	110	111
y	0	1	0	0	0	1	1	1
a SA0	0	1	0	0	0	1	0	0
a SA1	0	1	1	1	0	1	1	1

Stuck-at Faults

Στο παράδειγμά μας:

 1. Πόσα λάθη υπάρχουν;
2. Πώς επηρεάζει το καθένα;
3. Πώς μπορώ να τα ανακαλύψω όλα;

- # fault sites: $n=9$
- # single faults = $2 \times 9 = 18$




Truth table for fault-free behavior and behavior of all possible stuck-at faults

$x_1x_2x_3$	000	001	010	011	100	101	110	111
y	0	1	0	0	0	1	1	1
a SA0	0	1	0	0	0	1	0	0
a SA1	0	1	1	1	0	1	1	1
b SA0	0	1	0	1	0	1	0	1
b SA1	0	0	0	0	1	1	1	1
c SA0	0	0	0	0	0	0	1	1
c SA1	1	1	0	0	1	1	1	1
d SA0	0	1	0	0	0	1	0	0
d SA1	0	1	0	0	1	1	1	1
e SA0	0	1	0	1	0	1	1	1
e SA1	0	0	0	0	0	0	1	1
f SA0	0	0	0	0	0	0	1	1
f SA1	0	1	0	1	0	1	1	1
g SA0	0	1	0	0	0	1	0	0
g SA1	1	1	1	1	1	1	1	1
h SA0	0	0	0	0	0	0	1	1
h SA1	1	1	1	1	1	1	1	1
i SA0	0	0	0	0	0	0	0	0
i SA1	1	1	1	1	1	1	1	1

Stuck-at Faults

 - Διακρίνουμε “easy” και “hard” faults
- Hard faults:
 - f-SA1, e-SA0, d-SA1
- Easy faults:
 - g-SA1, h-SA1, i-SA0, i-SA1




Truth table for fault-free behavior and behavior of all possible stuck at faults

$x_1x_2x_3$	000	001	010	011	100	101	110	111
y	0	1	0	0	0	1	1	1
a SA0	0	1	0	0	0	1	0	0
a SA1	0	1	1	1	0	1	1	1
b SA0	0	1	0	1	0	1	0	1
b SA1	0	0	0	0	1	1	1	1
c SA0	0	0	0	0	0	0	1	1
c SA1	1	1	0	0	1	1	1	1
d SA0	0	1	0	0	0	1	0	0
d SA1	0	1	0	0	1	1	1	1
e SA0	0	1	0	1	0	1	1	1
e SA1	0	0	0	0	0	0	1	1
f SA0	0	0	0	0	0	0	1	1
f SA1	0	1	0	1	0	1	1	1
g SA0	0	1	0	0	0	1	0	0
g SA1	1	1	1	1	1	1	1	1
h SA0	0	0	0	0	0	0	1	1
h SA1	1	1	1	1	1	1	1	1
i SA0	0	0	0	0	0	0	0	0
i SA1	1	1	1	1	1	1	1	1

Stuck-at Faults

 - Ποια vectors πρέπει να πάρω οπωσδήποτε;
 - 011 για τα f-SA1, e-SA0
 - 100 για τα d-SA1
- Detect total of 10 faults
- 001 and 110 detect remaining 8 faults



Truth table for fault-free behavior and behavior of all possible stuck at faults

$x_1x_2x_3$	000	001	010	011	100	101	110	111
y	0	1	0	0	0	1	1	1
a SA0	0	1	0	0	0	1	0	0
a SA1	0	1	1	1	0	1	1	1
b SA0	0	1	0	1	0	1	0	1
b SA1	0	0	0	0	1	1	1	1
c SA0	0	0	0	0	0	0	1	1
c SA1	1	1	0	0	1	1	1	1
d SA0	0	1	0	0	0	1	0	0
d SA1	0	1	0	0	1	1	1	1
e SA0	0	1	0	1	0	1	1	1
e SA1	0	0	0	0	0	0	1	1
f SA0	0	0	0	0	0	0	1	1
f SA1	0	1	0	1	0	1	1	1
g SA0	0	1	0	0	0	1	0	0
g SA1	1	1	1	1	1	1	1	1
h SA0	0	0	0	0	0	0	1	1
h SA1	1	1	1	1	1	1	1	1
i SA0	0	0	0	0	0	0	0	0
i SA1	1	1	1	1	1	1	1	1

Transistor Faults


□ Ένα transistor μπορεί να έχει

τα εξής λάθη:

- Stuck-short
 - Also known as stuck-on
 - Άγει συνεχώς
- Stuck-open
 - Also known as stuck-off
 - Δεν άγει ποτέ

□ Παράδειγμα: Πύλη NOR

 - Reminder:
- P:
 - 0=> conduct,
 - 1=> no conduct
 - N:
 - 0: no conduct,
 - 1: conduct




Truth table for fault-free circuit

<i>AB</i>	00	01	10	11
<i>Z</i>	1	0	0	0

Transistor Fault effects

- Stuck-short faults cause conducting path from V_{DD} to V_{SS}
- Stuck-open faults cause output node to store last voltage level


**2-input CMOS
NOR gate**

 

Transistor Faults

□ Example circuit

 - 2-input CMOS NOR gate
- # fault sites: $n=4$
- # single faults = $2 \times 4 = 8$



Truth table for fault-free circuit and N_1 stuck-short transistor fault

AB	00	01	10	11
Z	1	0	0	0
N_1 stuck-short	I_{DDQ}	0	0	0


Truth table for fault-free circuit and N_1 stuck-open transistor fault

AB	00	01	10	11
Z	1	0	0	0
N_1 stuck-open	1	0	last Z	0

Transistor Faults

□ Example circuit

 - 2-input CMOS NOR gate
- # fault sites: $n=4$
- # single faults = $2 \times 4 = 8$




Truth table for fault-free circuit and all possible transistor faults

AB	00	01	10	11
Z	1	0	0	0
N_1 stuck-short	I_{DDQ}	0	0	0
N_2 stuck-short	I_{DDQ}	0	0	0
P_1 stuck-short	1	0	I_{DDQ}	0
P_2 stuck-short	1	I_{DDQ}	0	0

AB	00	01	10	11
Z	1	0	0	0
N_1 stuck-open	1	0	last Z	0
N_2 stuck-open	1	last Z	0	0
P_1 stuck-open	last Z	0	0	0
P_2 stuck-open	last Z	0	0	0

Transistor Faults

 - Τι πρέπει να κάνω για να ελέγξω το fault N1 stuck-short;
- Πόσα διανύσματα (συνδυασμούς εισόδων) χρειάζομαι;
- Τι πρέπει να κάνω για να ελέγξω το fault N1 stuck-open;
- Πόσα διανύσματα (συνδυασμούς εισόδων) χρειάζομαι;




Truth table for fault-free circuit and all possible transistor faults

<i>AB</i>	00	01	10	11
<i>Z</i>	1	0	0	0
N ₁ stuck-open	1	0	last Z	0
N ₁ stuck-short	I _{DDQ}	0	0	0
N ₂ stuck-open	1	last Z	0	0
N ₂ stuck-short	I _{DDQ}	0	0	0
P ₁ stuck-open	last Z	0	0	0
P ₁ stuck-short	1	0	I _{DDQ}	0
P ₂ stuck-open	last Z	0	0	0
P ₂ stuck-short	1	I _{DDQ}	0	0

Transistor Faults

 - Stuck-short faults cause conducting path from V_{DD} to V_{SS}
 - Can be detected by monitoring steady-state power supply current I_{DDQ}
- Stuck-open faults cause output node to store last voltage level
 - Requires sequence of 2 vectors for detection
 - 00 → 10 detects N_1 stuck-open




Truth table for fault-free circuit and all possible transistor faults

AB	00	01	10	11
Z	1	0	0	0
N_1 stuck-open	1	0	last Z	0
N_1 stuck-short	I_{DDQ}	0	0	0
N_2 stuck-open	1	last Z	0	0
N_2 stuck-short	I_{DDQ}	0	0	0
P_1 stuck-open	last Z	0	0	0
P_1 stuck-short	1	0	I_{DDQ}	0
P_2 stuck-open	last Z	0	0	0
P_2 stuck-short	1	I_{DDQ}	0	0

Transistor Faults

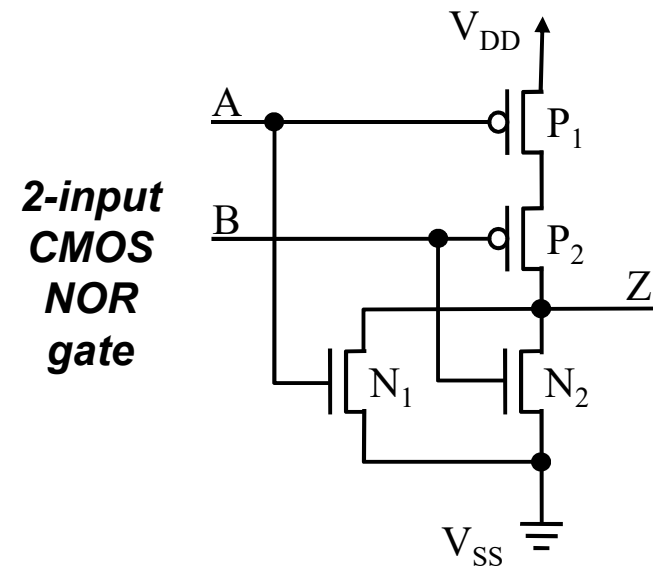- Τι πρέπει να κάνω για να ελέγξω όλα τα stuck-short λάθη;
- Πόσα διανύσματα (συνδυασμούς εισόδων) χρειάζομαι;
- Τι πρέπει να κάνω για να ελέγξω όλα τα stuck-open λάθη;
- Πόσα διανύσματα (συνδυασμούς εισόδων) χρειάζομαι;



Truth table for fault-free circuit and all possible transistor faults

<i>AB</i>	00	01	10	11
Z	1	0	0	0
N_1 stuck-open	1	0	last Z	0
N_1 stuck-short	I_{DDQ}	0	0	0
N_2 stuck-open	1	last Z	0	0
N_2 stuck-short	I_{DDQ}	0	0	0
P_1 stuck-open	last Z	0	0	0
P_1 stuck-short	1	0	I_{DDQ}	0
P_2 stuck-open	last Z	0	0	0
P_2 stuck-short	1	I_{DDQ}	0	0

Shorts and Opens

□ Wires can be

■ Open

– Opens in wires interconnecting transistors to form gates

- behave like transistor stuck-open faults

– Opens in wires interconnecting gates to form circuit

- behave like stuck-at faults

– Opens are detected by vectors detecting transistor and stuck-at faults

■ Short to an adjacent wire

– Also known as a bridging fault



Bridging Faults

Three different models

- Wired-AND/OR
- Dominant
- Dominant-AND/OR



Fault-free case

A_S B_S	0	0	0	1	1	0	1	1
A_D B_D	0	0	0	1	1	0	1	1

  



Wired-AND

Wired-OR

  



A dominates B

B dominates A

  

A dominant-AND B

A dominant-OR B

  

B dominant-AND A

B dominant-OR A



Bridging Faults

Three different models

- Wired-AND/OR
- Dominant
- Dominant-AND/OR



Detectable by I_{DDQ} testing

A_S B_S	0	0	0	1	1	0	1	1
A_D B_D	0	0	0	1	1	0	1	1
Wired-AND	0	0	0	0	0	0	1	1
Wired-OR	0	0	1	1	1	1	1	1
A dominates B	0	0	0	0	1	1	1	1
B dominates A	0	0	1	1	0	0	1	1
A dominant-AND B	0	0	0	0	1	0	1	1
B dominant-AND A	0	0	0	1	0	0	1	1
A dominant-OR B	0	0	0	1	1	1	1	1
B dominant-OR A	0	0	1	1	1	0	1	1

  



Wired-AND

Wired-OR

  



A dominates B

B dominates A

  

A dominant-AND B

A dominant-OR B

  


B dominant-AND A

B dominant-OR A


Delay Faults and Crosstalk

 - Path-delay fault model considers cumulative propagation delay through CUT
 - 2 test vectors create transition along path
 - Faulty circuit has excessive delay
- Delays and glitches can be caused by crosstalk between interconnect
 - due to inductance and capacitive coupling



Faults in RAMs

 - Pattern sensitive fault
 - Contents of memory cell is affected by contents of neighboring cells
- Coupling fault
 - Transition in contents of one memory cell causes change in contents of another cell
- Detected with specific memory test algorithms



Memory March Algorithms

- Consist of March elements
- Example: March C-
- March elements M0-M5

Test Algorithm March C-	March Test Sequence
M0	↓(w0);
M1	↑(r0, w1);
M2	↑(r1, w0);
M3	↓(r0, w1);
M4	↓(r1, w0);
M5	↑(r0)

Notation:

w0 = write 0 (or all 0's)

r1 = read 1 (or all 1's)

↑ = address up

↓ = address down

↕ = address either way

Coupling Faults

- Background Data Sequence (BDS) used for word-oriented memories

Test Algorithm	March Test Sequence
March C- w/o BDS	$\downarrow(w0)$; $\uparrow(r0, w1)$; $\uparrow(r1, w0)$; $\downarrow(r0, w1)$; $\downarrow(r1, w0)$; $\uparrow(r0)$
March C- with BDS	$\downarrow(w00)$; $\uparrow(r00, w11)$; $\uparrow(r11, w00)$; $\downarrow(r00, w11)$; $\downarrow(r11, w00)$; $\uparrow(r00)$ $\downarrow(w01)$; $\uparrow(r01, w10)$; $\uparrow(r10, w01)$; $\downarrow(r01, w10)$; $\downarrow(r10, w01)$; $\uparrow(r01)$

Notation:

w0 = write 0 (or all 0's)

r1 = read 1 (or all 1's)

\uparrow = address up

\downarrow = address down

\updownarrow = address either way

Overview of VLSI Test Technology


- Automatic Test Equipment (ATE) consists of:
 - Computer
 - for central control and flexible test & measurement for different products
 - Pin electronics & fixtures –
 - to apply test patterns to pins & sample responses
 - Test program –
 - controls timing of test patterns & compares response to known good responses
- Τι ανεβάζει την τιμή του tester?

Overview of VLSI Test Technology

- Automatic Test Pattern Generation (ATPG)
 - Algorithms generating sequence of test vectors for a given circuit based on specific fault models
- Fault simulation
 - Emulates fault models in CUT and applies test vectors to determine fault coverage
 - Simulation time (significant due to large number of faults to emulate)

Case study: ISCAS85 benchmarks

□ c17: toy benchmark

 

Test set:	Responses:
0111	0110
1010	
1100	
1011	
1100	0110

Πόσα διανύσματα χρειάζονται για να βρω όλα τα faults?

Overview of VLSI Test Technology


- Design for Testability (DFT)
 - Generally incorporated in design
 - Goal: improve controllability and/or observability of internal nodes of a chip or PCB

- Three basic approaches
 - Ad-hoc techniques
 - Scan design
 - Boundary Scan
 - Built-In Self-Test (BIST)


Design for Testability

□ Ad-hoc DFT techniques

 - Add internal test points (usually multiplexers) for
 - Controllability
 - Observability
- Added on a case-by-case basis
 - Primarily targets “hard to test” portions of chip



controllability test point

 

observability test point


Design for Testability

□ Scan design

- Transforms flip-flops of chip into a shift register
- Scan mode facilitates
 - Shifting in test vectors
 - Shifting out responses

□ Good CAD tool support

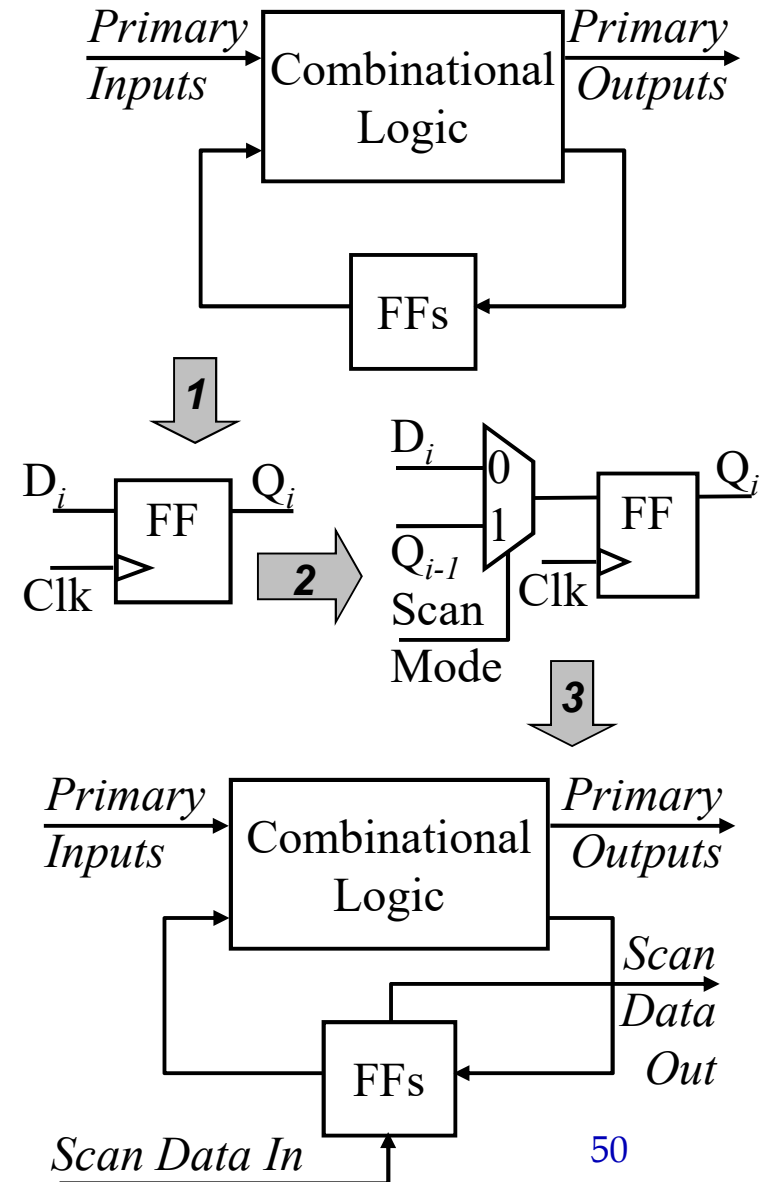
- Transforming flip-flops to shift register
- ATPG



Design for Testability

□ Boundary Scan – scan design applied to I/O buffers of chip

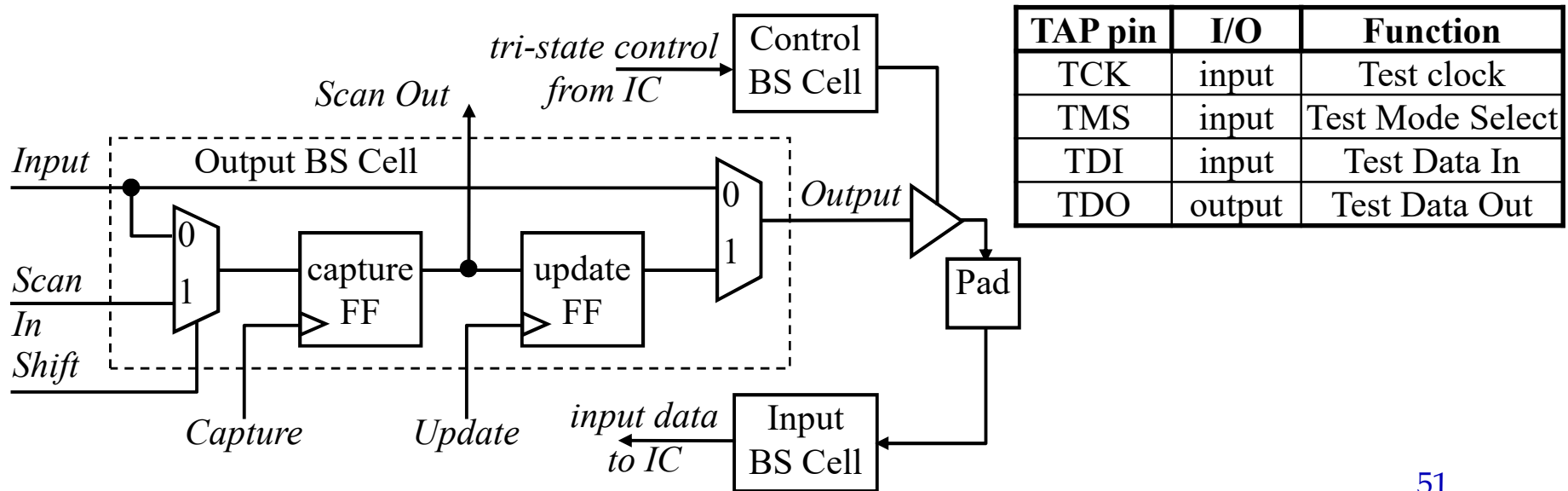
- Used for testing interconnect on PCB
 - Provides access to internal DFT capabilities
- IEEE standard 4-wire Test Access Port (TAP)



Design for Testability

□ Built-In Self-Test (BIST)

 - Incorporates test pattern generator (TPG) and output response analyzer (ORA) internal to design
 - Chip can test itself
- Can be used at all levels of testing
 - Device → PCB → system → field operation



Concluding Remarks

- Many new testing challenges presented by
 - Increasing size and complexity of embedded devices
 - Decreasing feature size
- Presented introduction to embedded systems testing

Thank you!

Questions?